Electronic Voting Machine

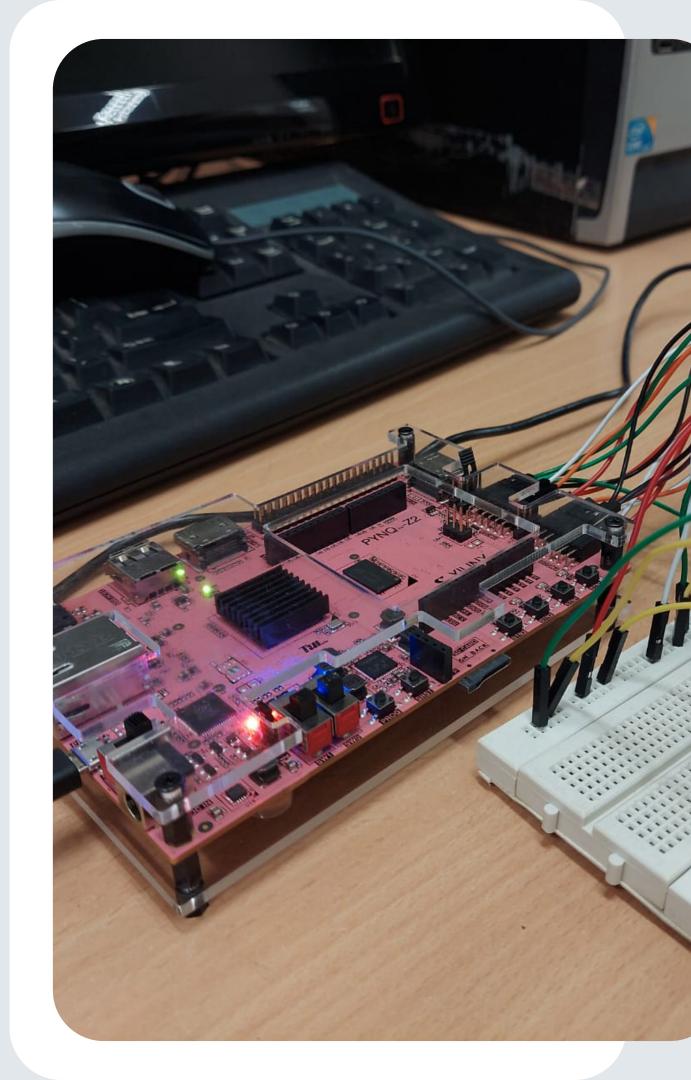


Table of Contents



Part 1:

Brief about EVM





Part 4:

Block Diagram





Part 2:

Details of our work





Part 5:

Logic and explaination





Part 3:

Implementation





Part 6:

FPGA board video



Brief about EVM

In this project, an Electronic Voting Machine (EVM) system is proposed which is in operation as transparent as the digital system. The Simplified Electronic Voting Machine (SEVM) responds on some flow of pulses coming from the switch operated by voter and produces the output of the counting values i.e. total casting votes of individual nominee and displays it. The machine is controlled both automatically and manually to operate the system for successive voters and to ensure that a voter can give only one vote to his/her chosen candidate of the same position




DETAILS OF OUR WORK - IMPLEMENTATION

Designed and implemented an electronic voting machine system that on the positive edge of the clock, checks if any of the buttons is pressed, if yes increases the count of votes of the candidate corresponding to the button, and blinks the LED in front of the candidate button. This entire functioning takes place only if the ballot is on. A Reset button to reset the counter of each candidate votes and a BCD to display the votes of each candidate turn by turn.

Major Functionalities

- Maximum 4 Candidates
- A ballot, Reset, display result button.
- Clock, BCD to display votes, etc.
- Buttons and LEDs correspond to each candidate.


Block Diagram

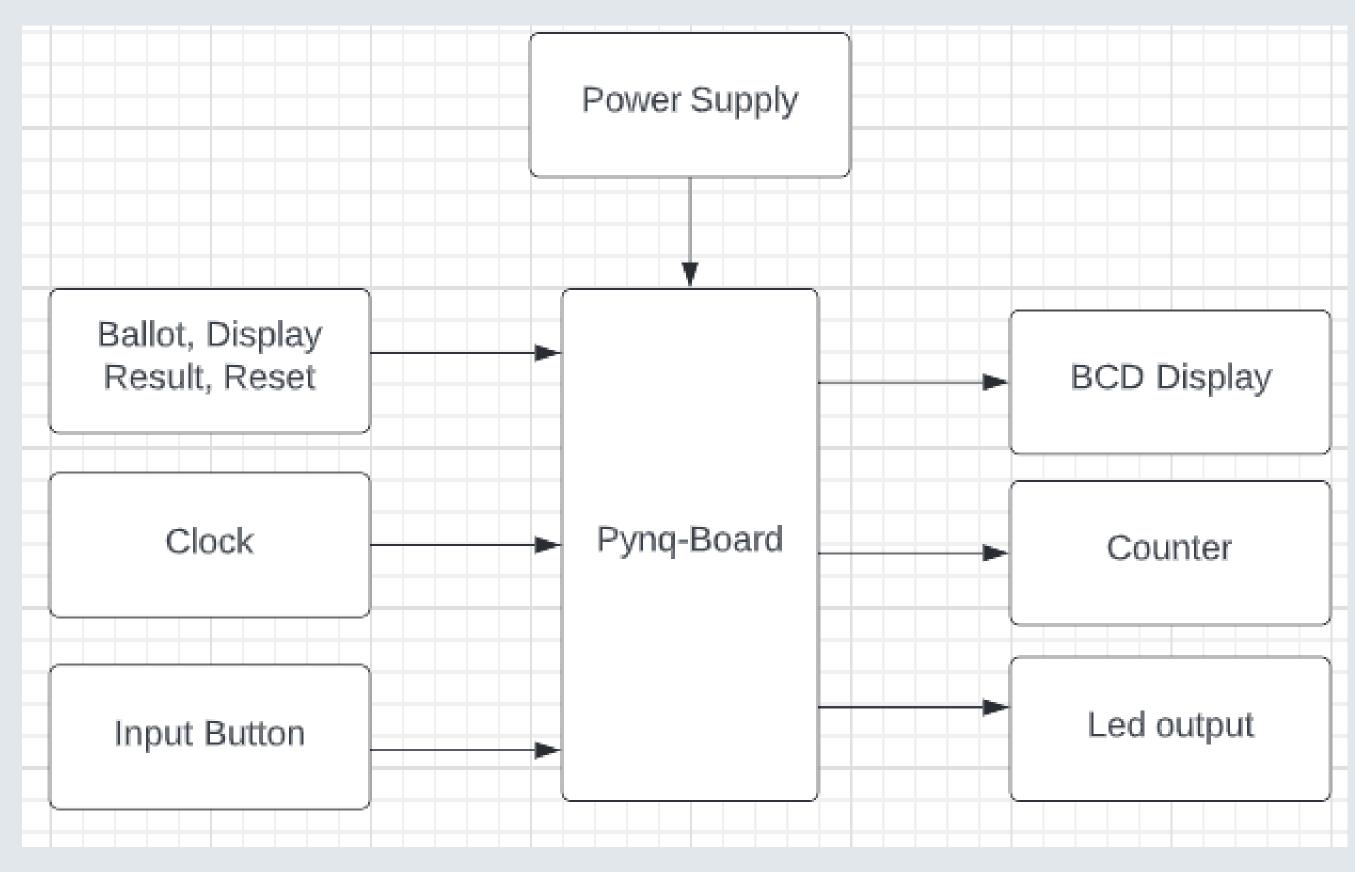


LOGIC AND EXPLANATION

- We tried to keep the logic simple so that it can be easily implemented and explained.
- We used 1 button and LED corresponding to each candidate, and a clock to regulate the counter of the button.
- A ballot as mentioned, to give controls to the host and a display result button, to show the output results on BCD moderated by selection buttons to select which count to show.
- A reset button to reset the count to zero.
- When reset is off and the ballot is on and let's say button 1 is pressed, then on the positive edge of the clock led 1 blinks, and counter 1 is increased by 1, same for every button, led and counter.
- When the display result is on, and the selection button i is on the court of votes for candidate i is shown.

Flow chart

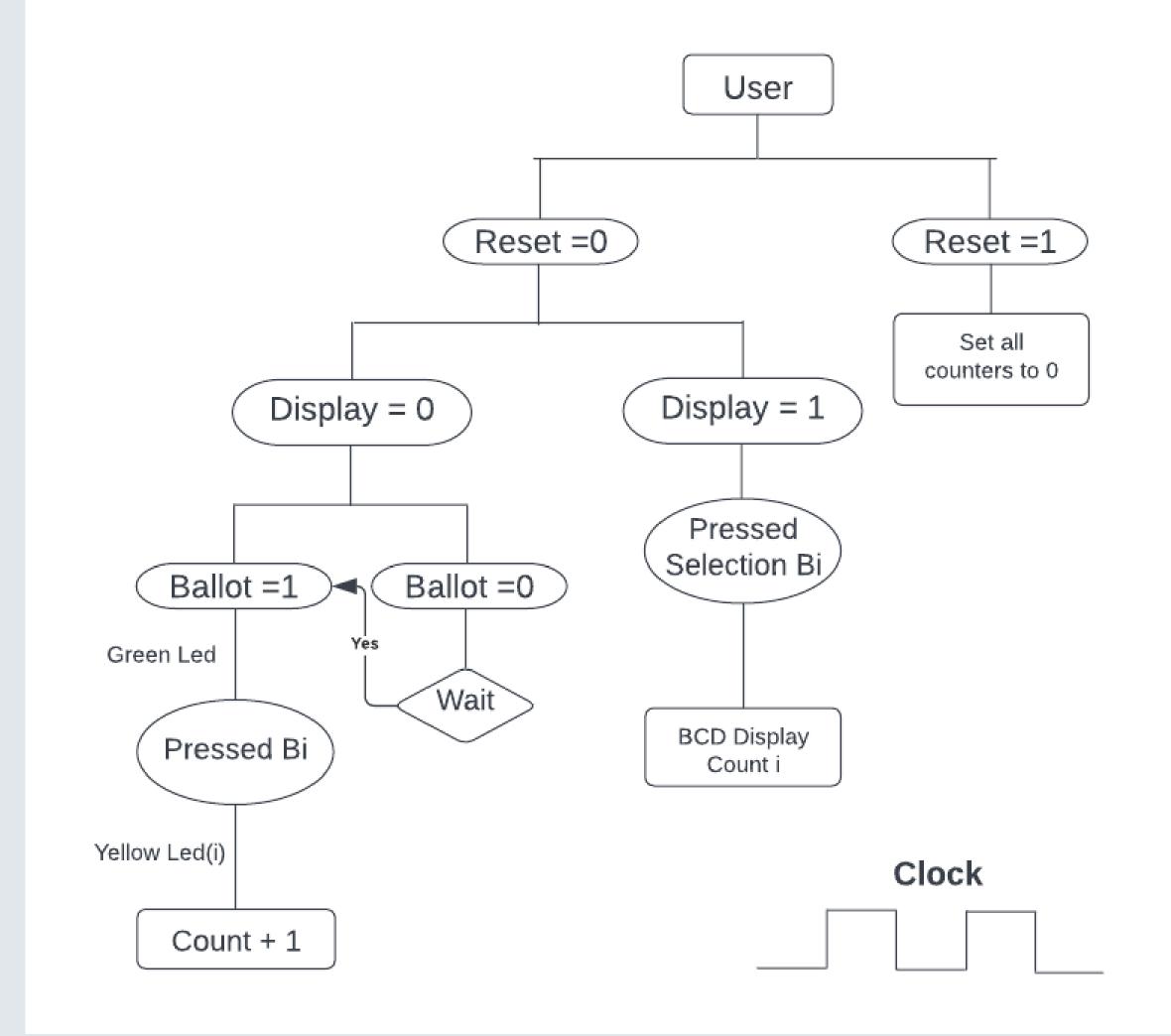

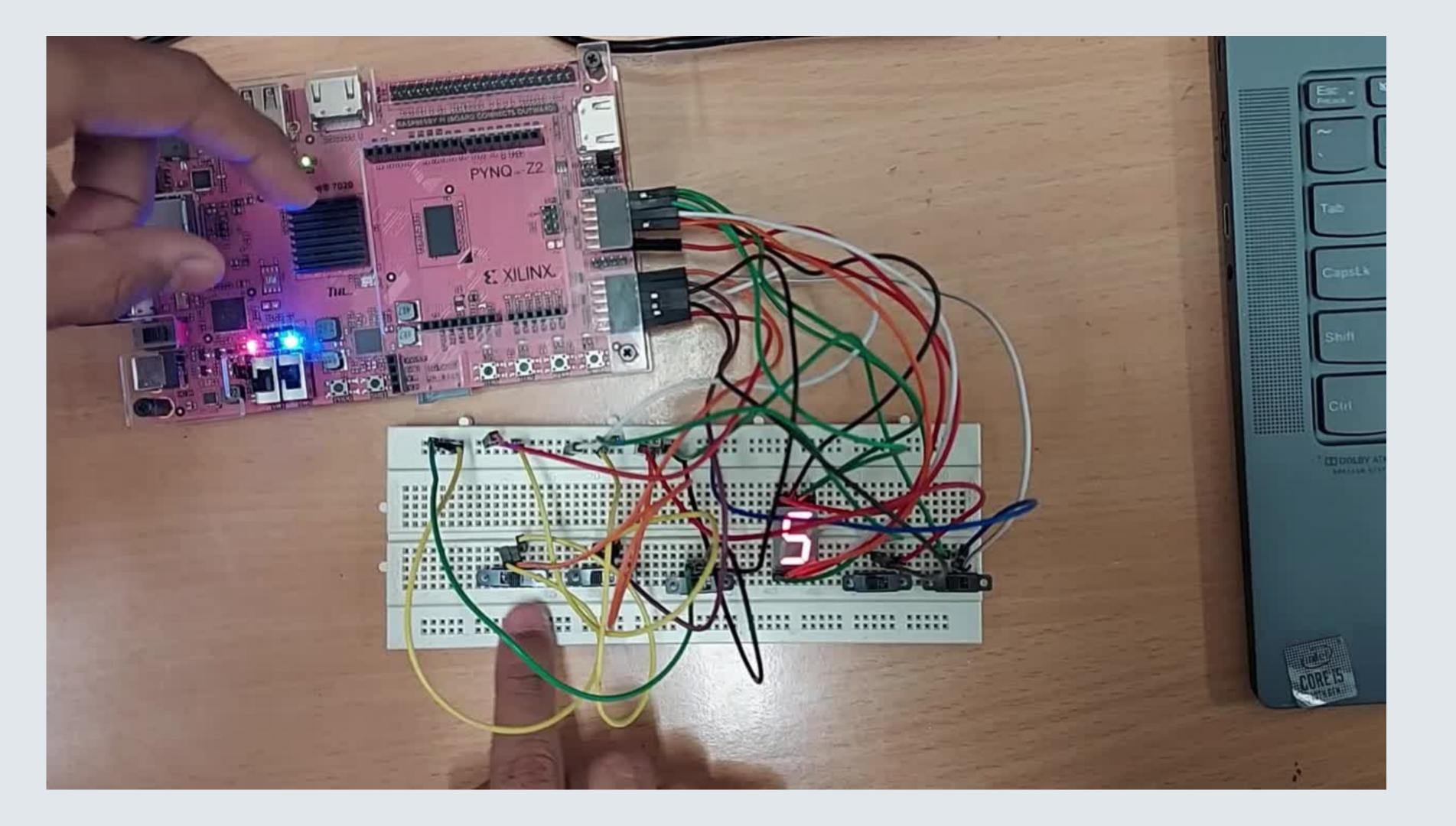

Code Snippet - EVM Module

```
module evm(clk,ballot,display_result,reset,b1,b2,b3,b4,selection_button_1,selection_button_2,selection_button_3,selection_button_4,green_led,l1,l2,l3,l4,cout_bcd_
input clk, ballot, display result;
input b1,b2,b3,b4,selection button 1,selection button 2,selection button 3,selection button 4,reset;
integer i;
output reg green led;
output reg 11;
output reg 12;
output reg 13;
output reg 14;
output co;
//output reg not voted;
reg [3:0] cout1;
reg [3:0] cout2;
reg [3:0] cout3;
reg [3:0] cout4;
reg temp ballot = 0;
output [6:0] cout bcd 1;
reg [27:0] count=0;
always@(posedge clk)
  count = count + 1;
// CLK DIV
assign co = count[26];
always @(posedge co)
    begin
        if (reset) begin
            cout1=0;
            cout2=0;
            cout3=0;
            cout4=0;
```

```
coucz-0,
    cout3=0;
                                                   end
    cout4=0;
                                                   else if (b3) begin
end
                                                       cout3=cout3+1;
else begin
                                                       13=1;
   if(display_result)begin
                                                       11=0;
        cout1=cout1+0;
                                                       12=0;
       cout2=cout2+0;
                                                       14=0;
        cout3=cout3+0;
                                                   end
        cout4=cout4+0;
                                                   else if (b4) begin
    end
                                                       cout4=cout4+1;
    else begin
                                                       14=1;
       if(ballot)begin
                                                       11=0;
       green_led=1;
                                                       12=0;
           if(b1 & clk) begin
                                                       13=0;
                cout1=cout1+1;
                                                   end
                $display("%b",cout1);
                                                   else begin
               11=1;
                                                       11=0;
               12=0;
                                                       12=0;
               13=0;
                                                       13=0;
                14=0;
                                                       14=0;
            end
                                                   end
            else if (b2) begin
                                               end
                cout2=cout2+1;
                                               else begin
               12=1;
                                                   11=0;
                11=0;
                                                   12=0;
               13=0;
                                                   13=0;
                14=0;
                                                   14=0;
                                                   green_led=0;
            end
            else if (b3) begin
                                               end
```


```
else if (b4) begin
                       cout4=cout4+1;
                       14=1;
                       11=0;
                       12=0;
                       13=0;
                   end
                   else begin
                       11=0;
                       12=0;
                       13=0;
                       14=0;
                   end
               end
               else begin
                   11=0;
                   12=0;
                   13=0;
                   14=0;
                   green_led=0;
               end
           end
       end
   end
display_select disp1(display_result,cout1,cout2,cout3,cout4,cout_bcd_1,selection_button_1,selection_button_2,selection_button_3,selection_button_4);
endmodule
```


Code Snippet - Display Select Module

```
module display select(display result, cin1, cin2, cin3, cin4, cout bcd, selection button 1, selection button 2, selection button 3, selection button 4);
input [3:0] cin1;
input [3:0] cin2;
input [3:0] cin3;
input [3:0] cin4;
output reg [6:0] cout bcd;
input display result, selection button 1, selection button 2, selection button 3, selection button 4;
always @(display result or selection button 1 or selection button 2 or selection button 3 or selection button 4)
begin
    if (display result) begin
        if (selection button 1) begin
            case(cin1)
            0: cout bcd=7'b1111110;1: cout bcd=7'b0110000;2: cout bcd=7'b1101101;3: cout bcd=7'b11111001;
            4: cout bcd=7'b0110011;5: cout bcd=7'b1011011;6: cout bcd=7'b1011111;7: cout bcd=7'b1110000;
            8: cout bcd=7'b1111111;9: cout bcd=7'b1111011;
            default: cout bcd=7'b0000000;
          endcase
          cout bcd=~cout bcd;
        end
        else if (selection button 2) begin
            case(cin2)
                0: cout bcd=7'b11111110;1: cout bcd=7'b0110000;2: cout bcd=7'b1101101;3: cout bcd=7'b11111001;
                4: cout bcd=7'b0110011;5: cout bcd=7'b1011011;6: cout bcd=7'b1011111;7: cout bcd=7'b1110000;
                8: cout bcd=7'b1111111;9: cout bcd=7'b1111011;
                default: cout bcd=7'b0000000;
              endcase
              cout bcd=~cout bcd;
        end
```

```
else if (selection button 3) begin
            case(cin3)
                0: cout_bcd=7'b1111110;1: cout_bcd=7'b0110000;2: cout_bcd=7'b1101101;3: cout_bcd=7'b11111001;
                4: cout_bcd=7'b0110011;5: cout_bcd=7'b1011011;6: cout_bcd=7'b1011111;7: cout_bcd=7'b1110000;
                8: cout_bcd=7'b1111111;9: cout_bcd=7'b1111011;
                default: cout bcd=7'b00000000;
              endcase
              cout bcd=~cout bcd;
        end
        else if (selection_button_4) begin
            case(cin4)
                0: cout_bcd=7'b11111110;1: cout_bcd=7'b01100000;2: cout_bcd=7'b1101101;3: cout_bcd=7'b11111001;
                4: cout_bcd=7'b0110011;5: cout_bcd=7'b1011011;6: cout_bcd=7'b1011111;7: cout_bcd=7'b1110000;
                8: cout_bcd=7'b1111111;9: cout_bcd=7'b1111011;
                default: cout bcd=7'b0000000;
              endcase
              cout bcd=~cout bcd;
        end
        else begin
            cout_bcd = 7'b0000001;
        end
    end
    else begin
        cout bcd = 7'b0000001;
    end
end
endmodule
```

Behind The Scenes

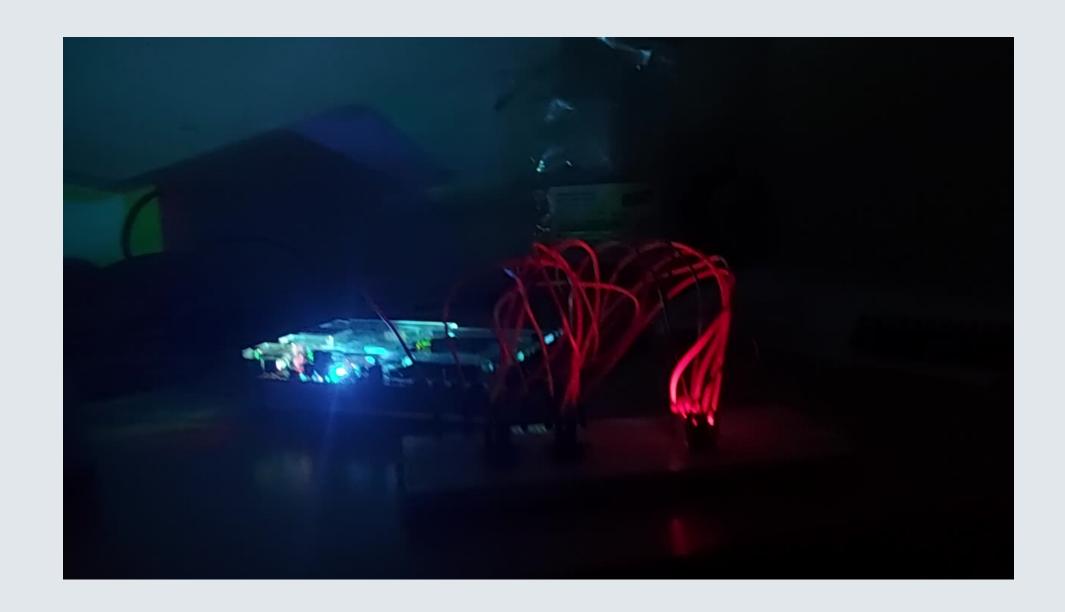

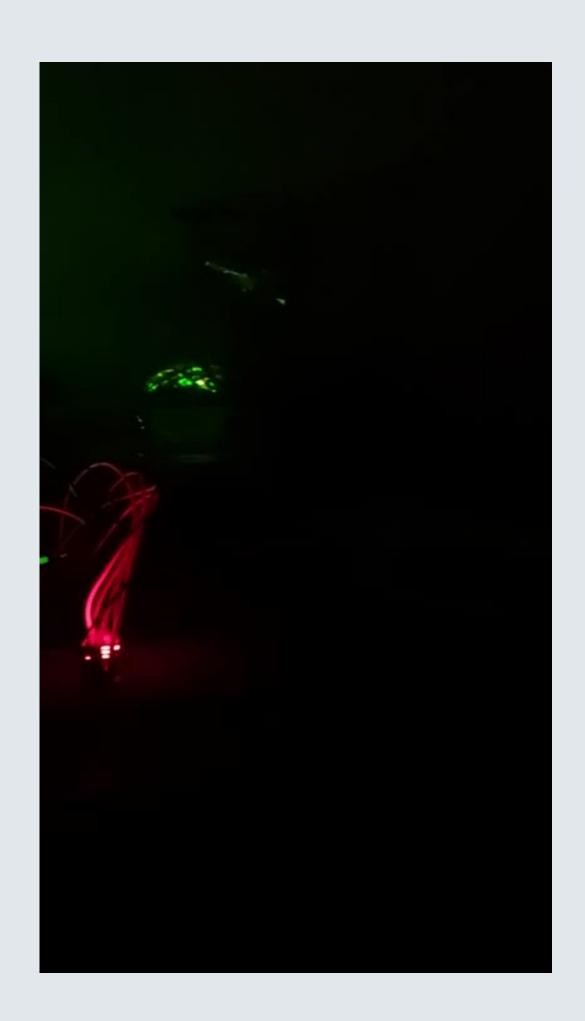

Thank you!